

 



The diagram illustrates the multiplication of two 5-bit binary numbers: 10110 (decimal 22) and 01101 (decimal 13). The numbers are aligned at the bottom of the grid. The first row shows the numbers with blue brackets above them labeled '22' and '13'. The second row shows the partial products: 101100 (cyan), 10110 (red), and 10110 (red). The asterisk (*) is placed between the two numbers.

						1	0	1	1	0		1	*		0	1	1	0	1
						1	0	1	1	0		0							
					1	0	1	1	0			1							
			1	0	1	1	0					1							
		1	0	1	1	0						0							
											0								

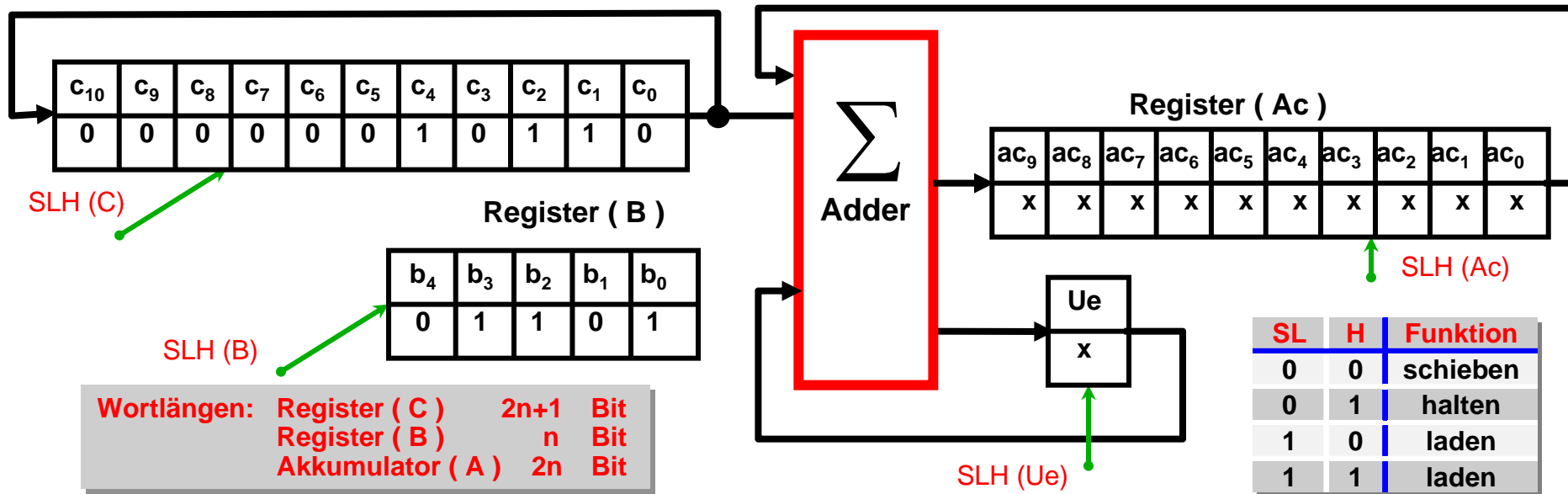


						22											13				
						1	0	1	1	0		1	*		0	1	1	0	1		
					1	0	1	1	0	0											
			1	0	1	1	0														
		1	0	1	1	0															
					0	1	1	1	1	0											

 


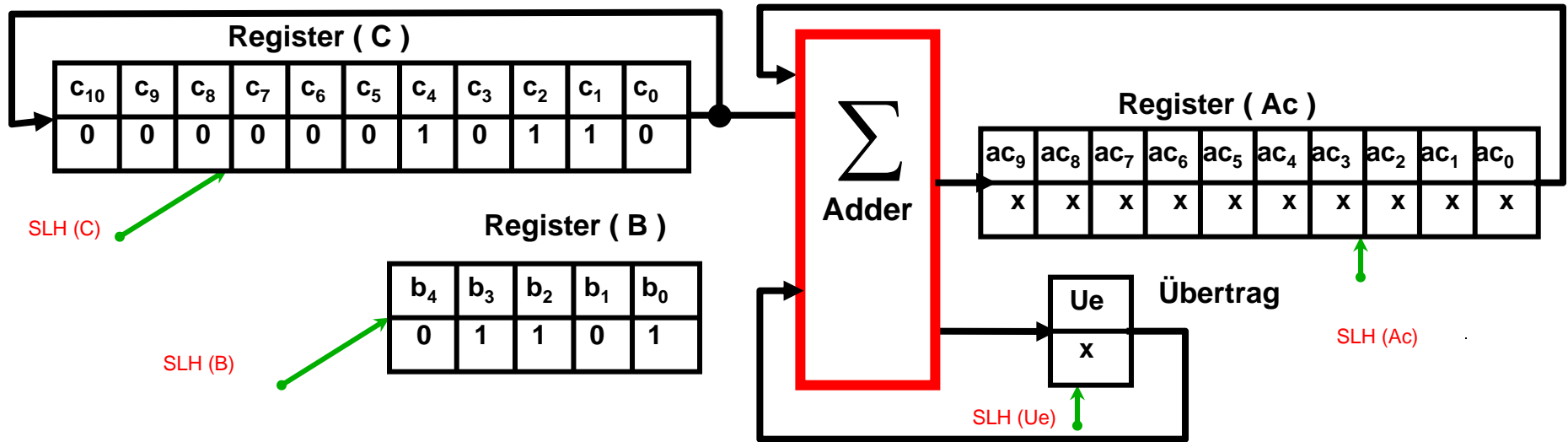


Befehl	SLH (C) (schieben)	<C>	SLH (B) (schieben)		SLH (Ac) (schieben)	<Ac>	Bemerkung
0	0	0000010110	0	01101	0	xxxxxxxxxx	Laden der Register

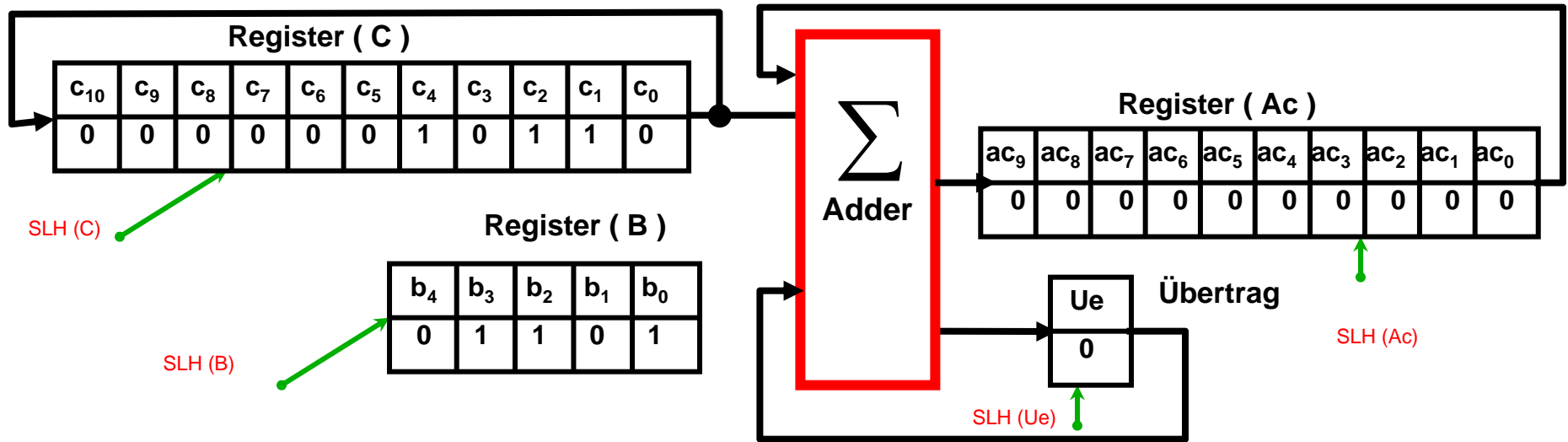


Befehl	SLH (C) (schieben)	<C>	SLH (B) (schieben)		SLH (Ac) (schieben)	<Ac>	Bemerkung
0	0	00000010110	0	01101	0	xxxxxxxxxxx	Laden der Register
1	0	00000010110	0	01101	0	0000000000	Lösche AC

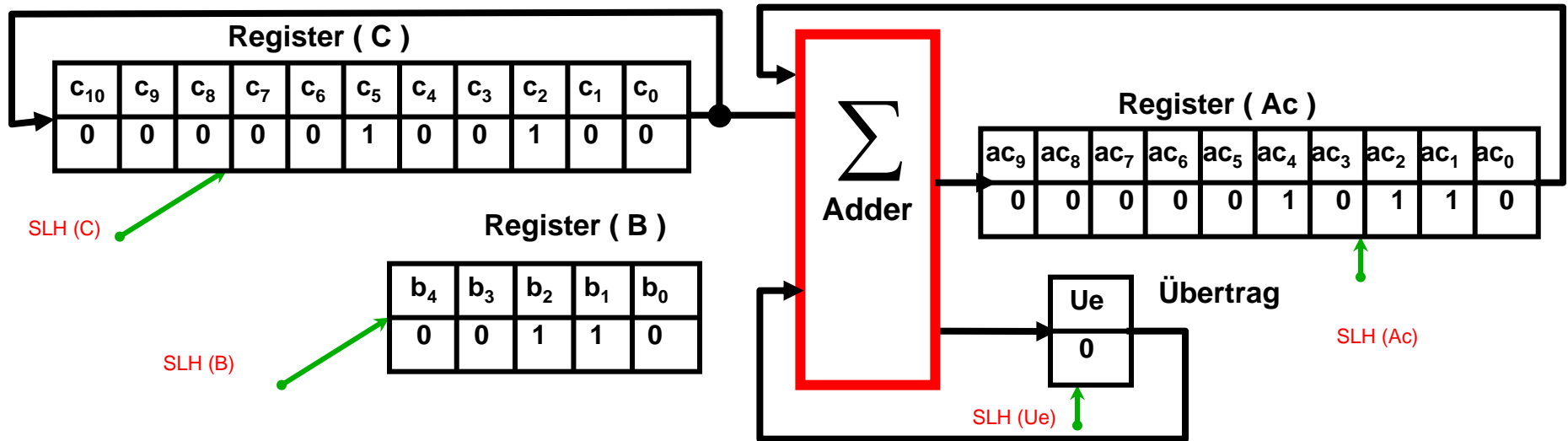


Befehl	SLH (C) (schieben)	<C>	SLH (B) (schieben)		SLH (Ac) (schieben)	<Ac>	Bemerkung
0	0	00000010110	0	01101	0	xxxxxxxxxxx	Laden der Register
1	0	00000010110	0	01101	0	0000000000	Lösche AC
2	10	00000101100	1	00110	10	0000010110	1. Addition

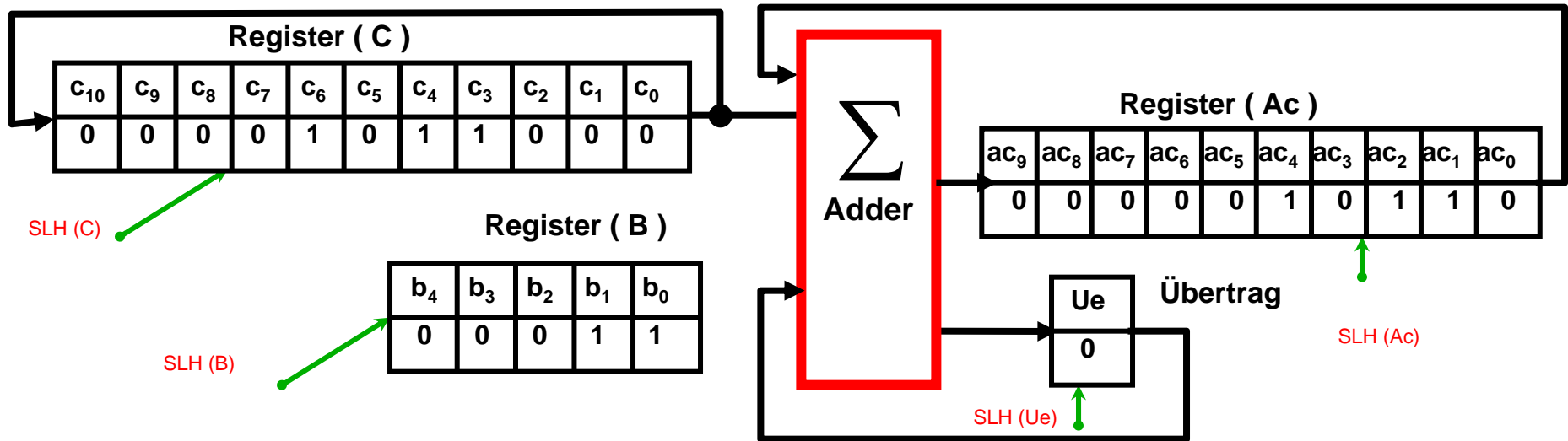


Befehl	SLH (C) (schieben)	<C>	SLH (B) (schieben)		SLH (Ac) (schieben)	<Ac>	Bemerkung
0	0	00000010110	0	01101	0	xxxxxxxxxxx	Laden der Register
1	0	00000010110	0	01101	0	0000000000	Lösche AC
2	10	00000101100	1	00110	10	0000010110	1. Addition
3	10	00001011000	1	00011	0	0000010110	

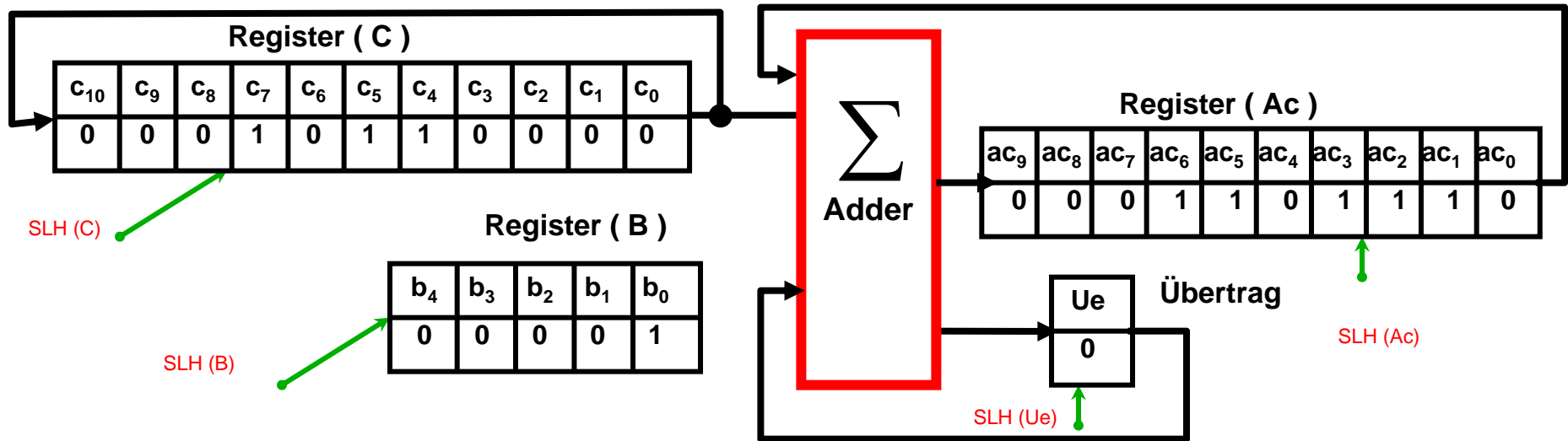


Befehl	SLH (C) (schieben)	<C>	SLH (B) (schieben)		SLH (Ac) (schieben)	<Ac>	Bemerkung
0	0	00000010110	0	01101	0	xxxxxxxxxxx	Laden der Register
1	0	00000010110	0	01101	0	0000000000	Lösche AC
2	10	00000101100	1	00110	10	0000010110	1. Addition
3	10	00001011000	1	00011	0	0000010110	
4	10	00010110000	1	00001	10	0001101110	2. Addition

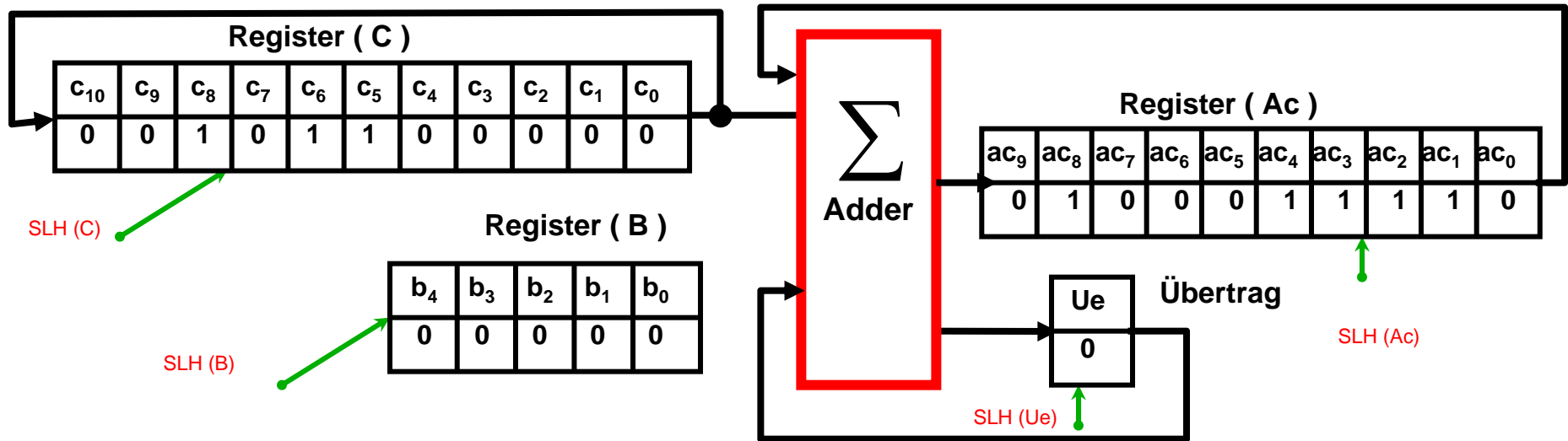

Befehl	SLH (C) (schieben)	<C>	SLH (B) (schieben)		SLH (Ac) (schieben)	<Ac>	Bemerkung
0	0	00000010110	0	01101	0	xxxxxxxxxxx	Laden der Register
1	0	00000010110	0	01101	0	0000000000	Lösche AC
2	10	00000101100	1	00110	10	0000010110	1. Addition
3	10	00001011000	1	00011	0	0000010110	
4	10	00010110000	1	00001	10	0001101110	2. Addition
5	10	00101100000	1	00000	10	0100011110	3. Addition
							Fertig

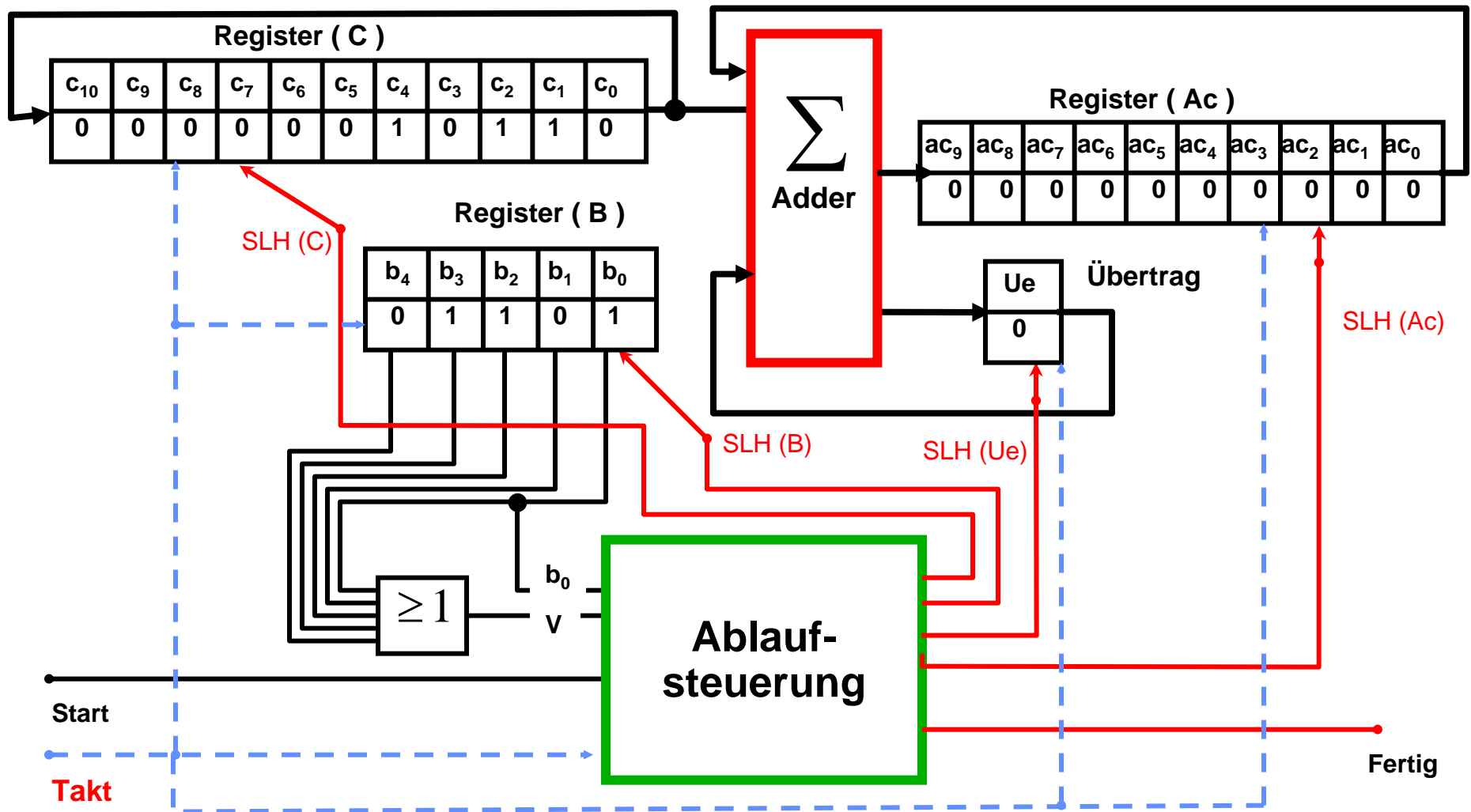

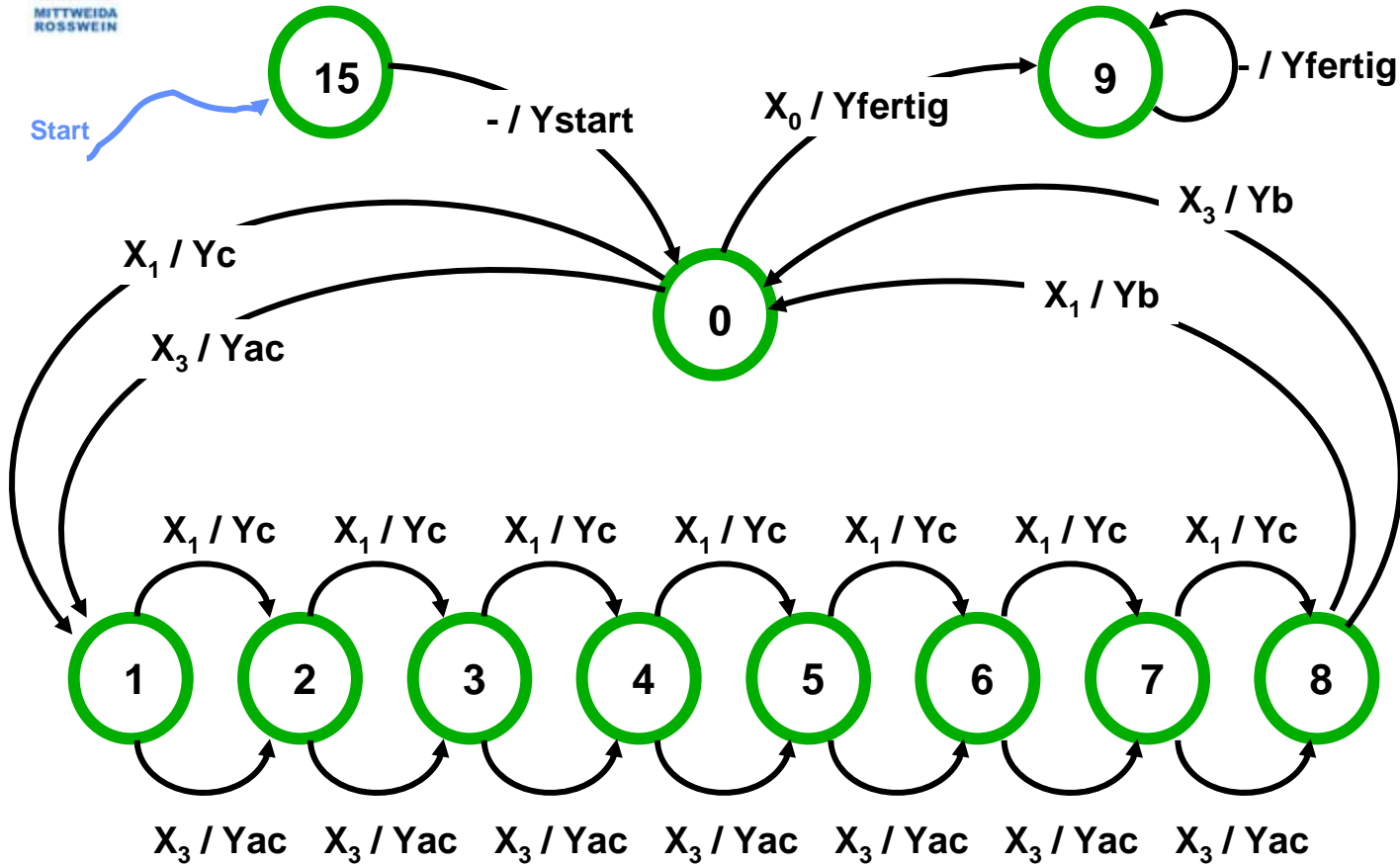


Start durch statisches Setzen aller FF's (Z_{15})

Schaltbedingung:
aktive Schaltflanke am
Takt

X	[b0, V]	
X0	0	0
X1	0	1
X2	1	0
X3	1	1

Z	[q3,q2,q1,q0]			
Z0	0	0	0	0
Z1	0	0	0	1
:	:	:	:	:
Z15	1	1	1	1

Y	[fertig, sl, halta, haltb, haltc]					
Yfertig	1	0	1	1	1	„ Fertiganzeige
Ystart	0	1	1	1	1	„ alle Reg. laden
Yb	0	0	1	0	1	„ schieben Reg b
Yc	0	0	1	1	0	„ schieben Reg c
Yac	0	0	0	1	0	„ schieben Reg a+c

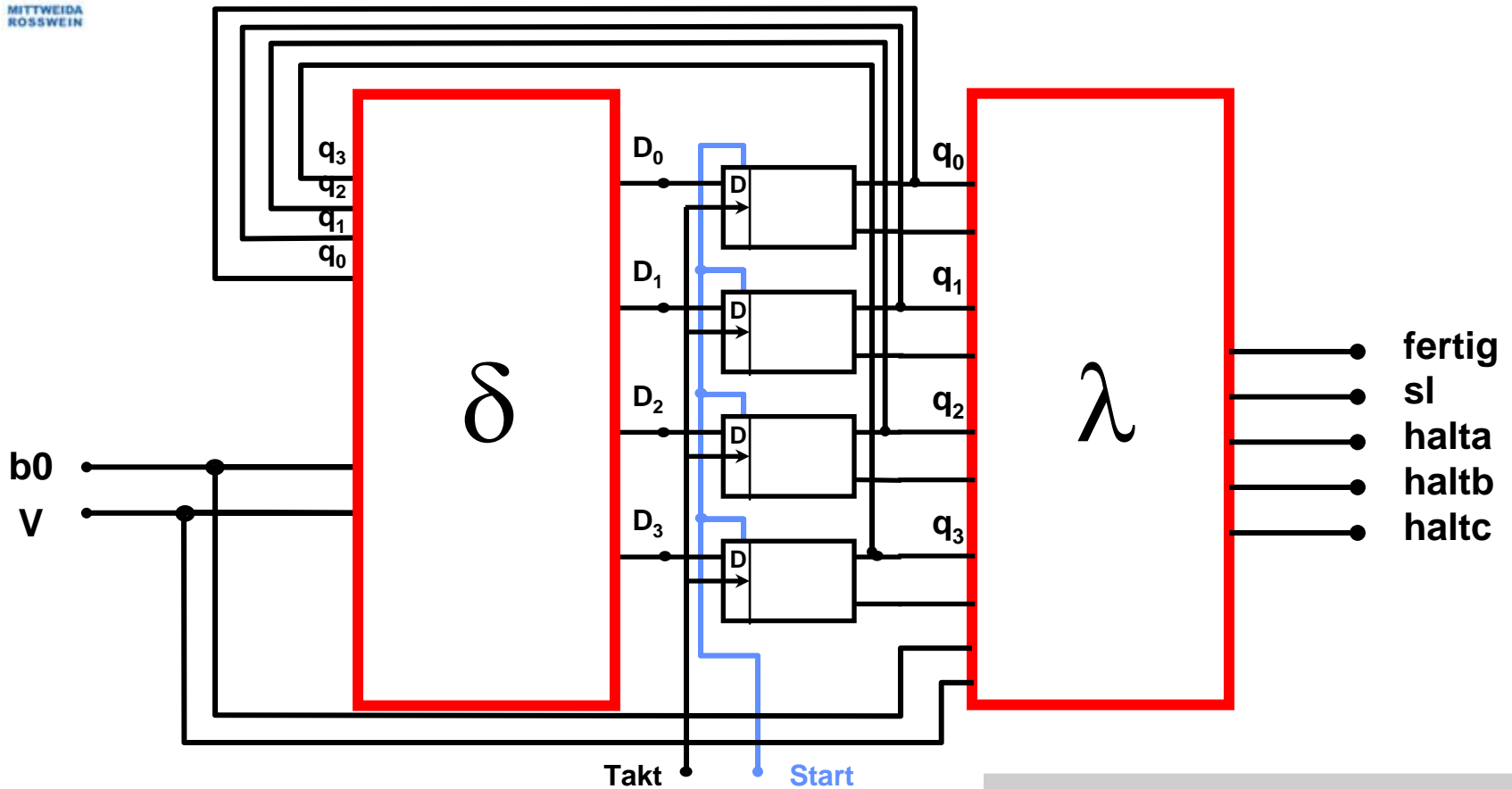

X	[b0, V]	
X0	0	0
X1	0	1
X2	1	0
X3	1	1

Z	[q3,q2,q1,q0]			
Z0	0	0	0	0
Z1	0	0	0	1
:	:	:	:	:
Z15	1	1	1	1

Y	[fertig, sl, halta, haltb, haltc]				
Yfertig	1	0	1	1	1
Ystart	0	1	1	1	1
Yb	0	0	1	0	1
Yc	0	0	1	1	0
Yac	0	0	0	1	0


U	b0	V	q3	q2	q1	q0	T3	T2	T1	T0	F	sl	ha	hb	hc
0	0	0	0	0	0	0									
9	0	0	1	0	0	1									
15	0	0	1	1	1	1									
16	0	1	0	0	0	0									
17	0	1	0	0	0	1									
18	0	1	0	0	1	0									
19	0	1	0	0	1	1									
20	0	1	0	1	1	0									
21	0	1	0	1	1	0									
22	0	1	0	1	1	0									
23	0	1	0	1	1	1									
24	0	1	1	0	0	0									
25	0	1	1	0	0	1									
31	1	1	1	1	1	1									
48	1	1	0	0	0	0									
49	1	1	0	0	0	1									

X [b0, V]

X0	0	0
X1	0	1
X2	1	0
X3	1	1

T q^{t+1}

0	q ^t
1	!q ^t

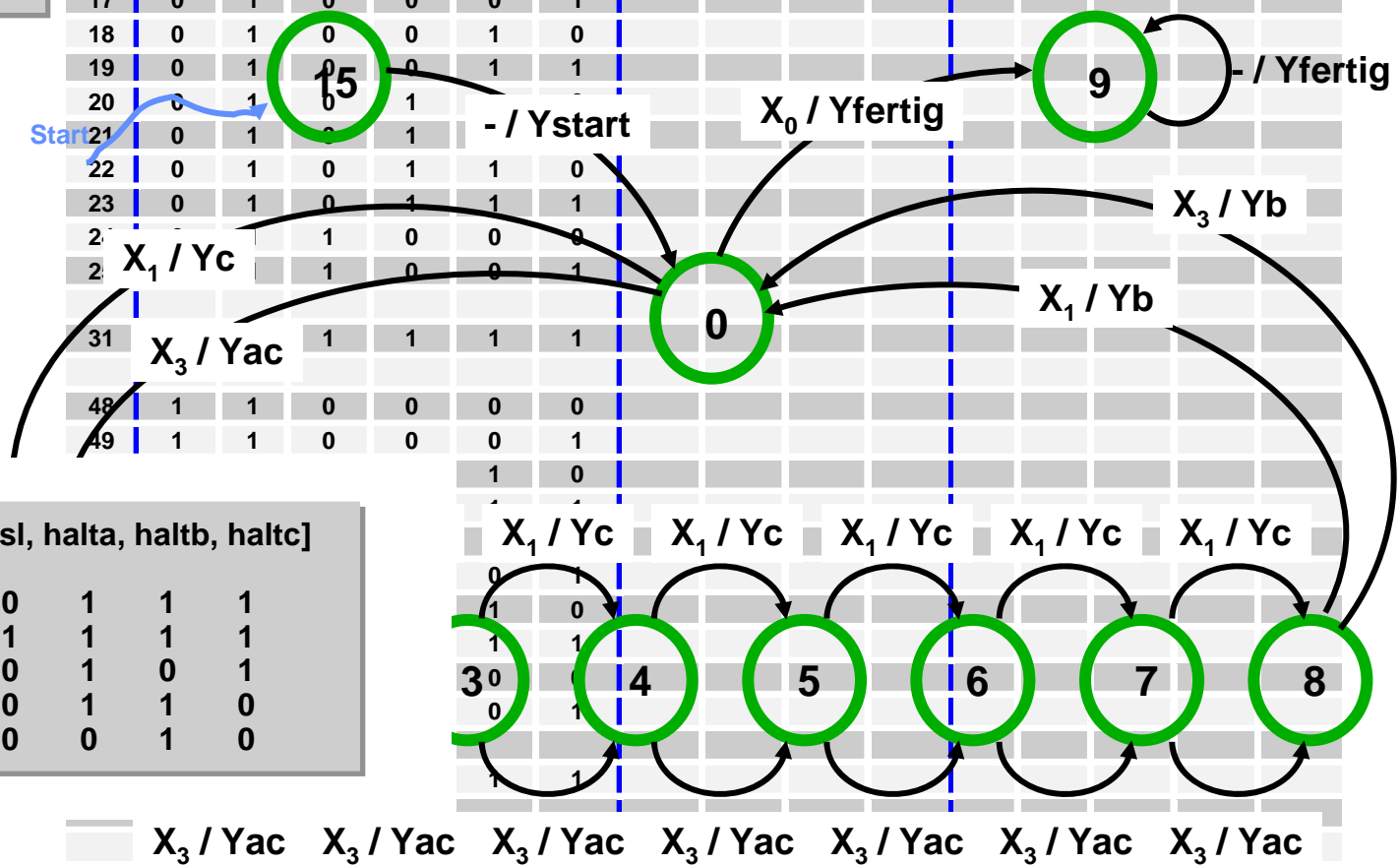


Y [fertig, sl, halta, haltb, haltc]


Yfertig	1	0	1	1	1
Ystart	0	1	1	1	1
Yb	0	0	1	0	1
Yc	0	0	1	1	0
Yac	0	0	0	1	0

U	b0	V	q3	q2	q1	q0	T3	T2	T1	T0	F	sl	ha	hb	hc
0	0	0	0	0	0	0	1	0	0	1	1	0	1	1	1
9	0	0	1	0	0	1	0	0	0	0	1	0	1	1	1
15	0	0	1	1	1	1	1	1	1	1	0	1	1	1	1
16	0	1	0	0	0	0	0	0	0	1	0	0	1	1	0
17	0	1	0	0	0	1	0	0	1	1	0	0	1	1	0
18	0	1	0	0	1	0	0	0	0	1	0	0	1	1	0
19	0	1	0	0	1	1	0	1	1	1	0	0	1	1	0
20	0	1	0	1	0	0	0	0	0	1	0	0	1	1	0
21	0	1	0	1	0	1	0	0	1	1	0	0	1	1	0
22	0	1	0	1	1	0	0	0	0	1	0	0	1	1	0
23	0	1	0	1	1	1	1	1	1	1	0	0	1	1	0
24	0	1	1	0	0	0	1	0	0	0	0	0	1	0	1
25	0	1	1	0	0	1	0	0	0	0	0	1	1	1	1
31	0	1	1	1	1	1	1	1	1	1	0	1	1	1	1
48	1	1	0	0	0	0	0	0	0	1	0	0	0	1	0
49	1	1	0	0	0	1	0	0	1	1	0	0	0	1	0
50	1	1	0	0	1	0	0	0	0	1	0	0	0	1	0
51	1	1	0	0	1	1	0	1	1	1	0	0	0	1	0
52	1	1	0	1	0	0	0	0	0	1	0	0	0	1	0
53	1	1	0	1	0	1	0	0	1	1	0	0	0	1	0
54	1	1	0	1	1	0	0	0	0	1	0	0	0	1	0
55	1	1	0	1	1	1	1	1	1	1	0	0	0	1	0
56	1	1	1	0	0	0	1	0	0	0	0	0	1	0	1
57	1	1	1	0	0	1	0	0	0	0	1	0	1	1	1
63	1	1	1	1	1	1	1	1	1	1	0	1	1	1	1
sonst							-	-	-	-	-	-	-	-	-

gleichgültig

 

gleichgültig

 


$$T3 = (q3 * !q0) v$$


$$(!v * !q3) v$$

$$(q2 * q1 * q0)$$


gleichgültig

 


gleichgültig

 


gleichgültig

 


gleichgültig

 

gleichgültig

 


gleichgütig

 


$$T0 = \boxed{!q3} \vee \boxed{q1}$$


gleichgültig

 


gleichgültig

 


gleichgültig

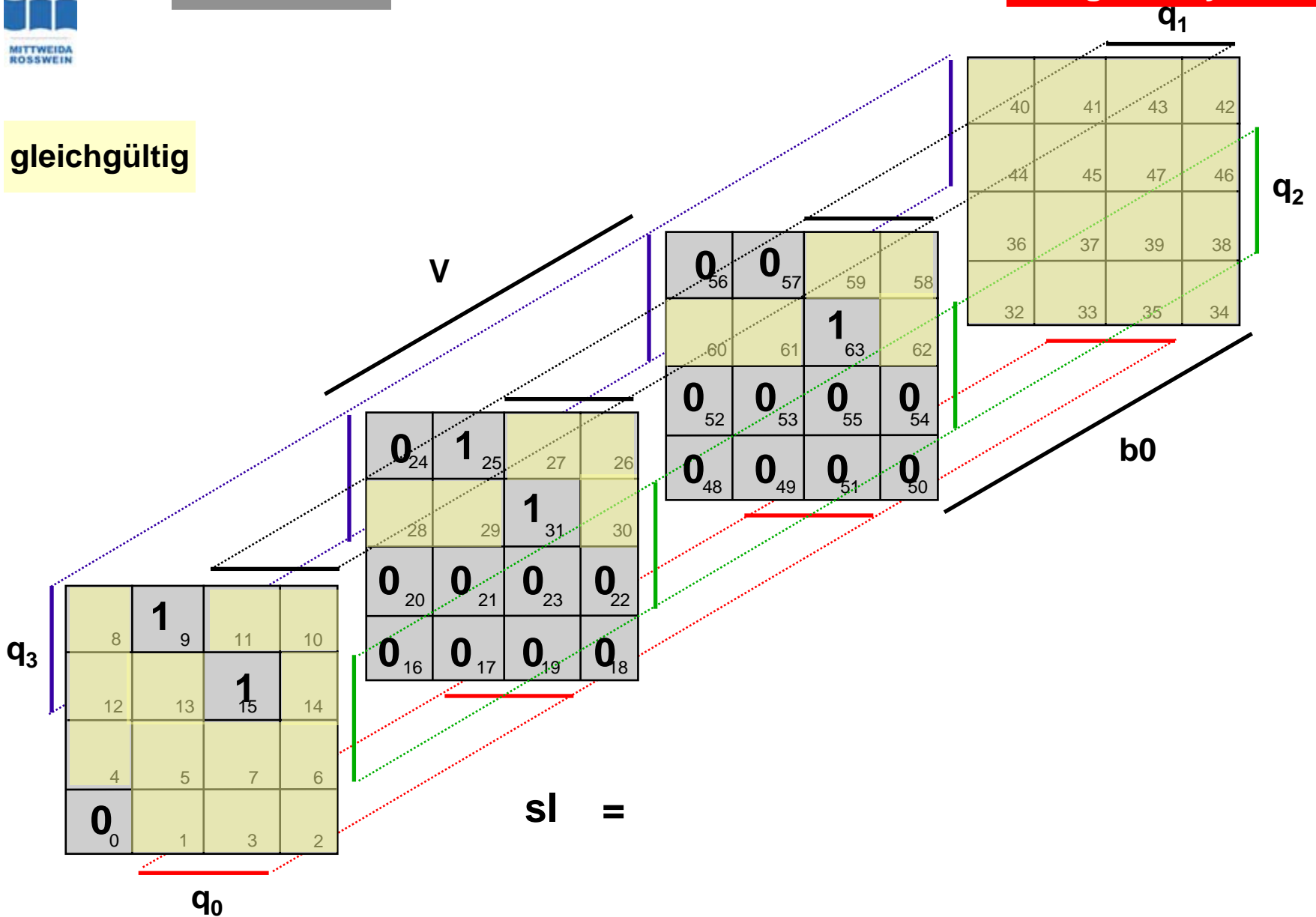


gleichgültig

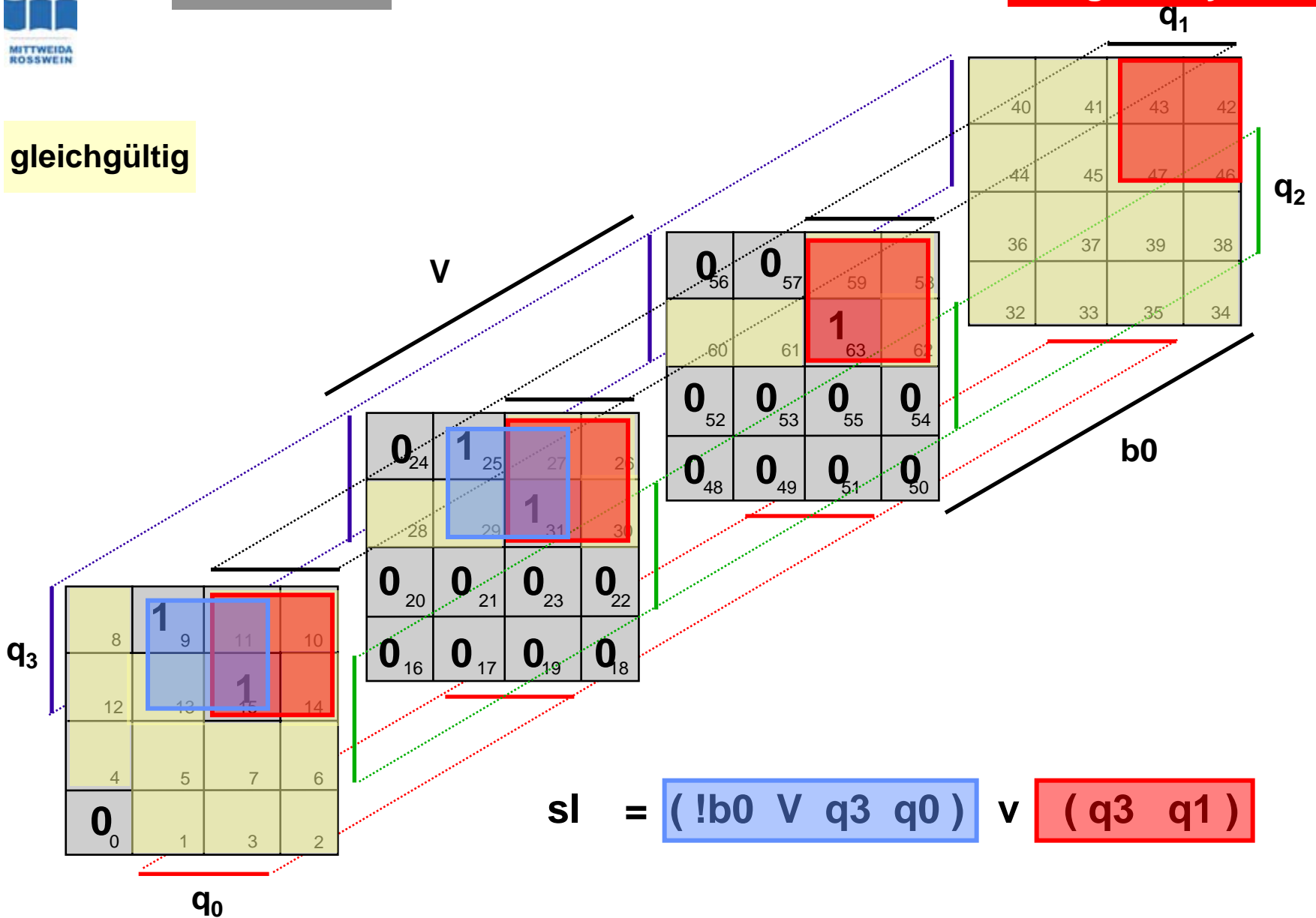


gleichgültig

 


gleichgültig

 


gleichgültig

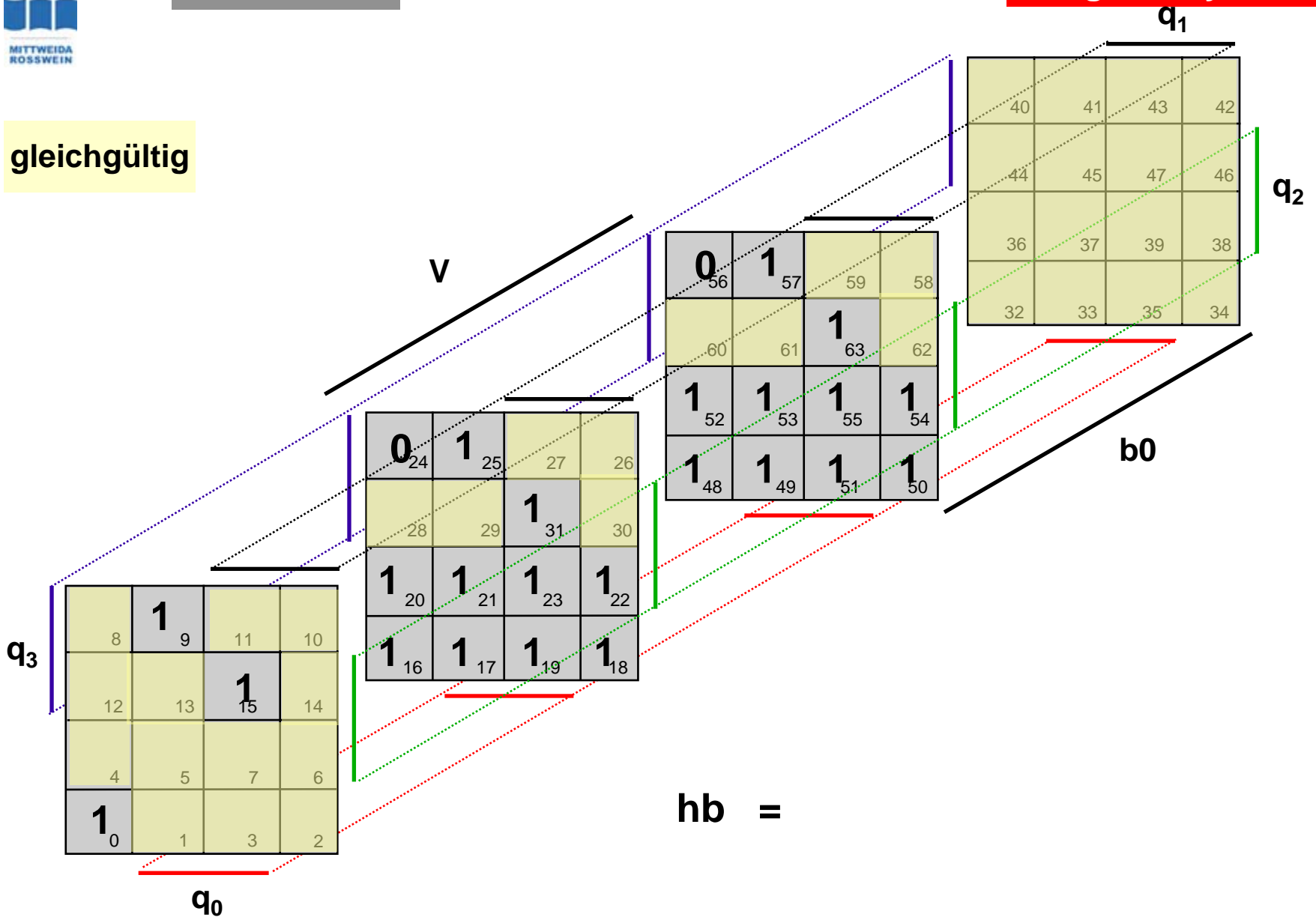


gleichgütig

 

gleichgültig

 

gleichgültig

 

$$T_3 = q_3 \bar{q}_0 \vee \bar{V} \bar{q}_3 \vee q_2 q_1 q_0$$

$$T_2 = q_1 q_0$$

$$T_1 = \bar{q}_3 q_0 \vee q_1 q_0$$

$$T_0 = \bar{q}_3 \vee q_1$$


$$F = b_0 q_3 \bar{q}_1 q_0 \vee \bar{V} \bar{q}_1$$


$$sl = \bar{b}_0 q_3 q_0 \vee q_3 q_1$$


$$ha = \bar{b}_0 \vee q_3$$


$$hb = \bar{q}_3 \vee q_0$$

$$hc = \bar{V} \vee q_3$$

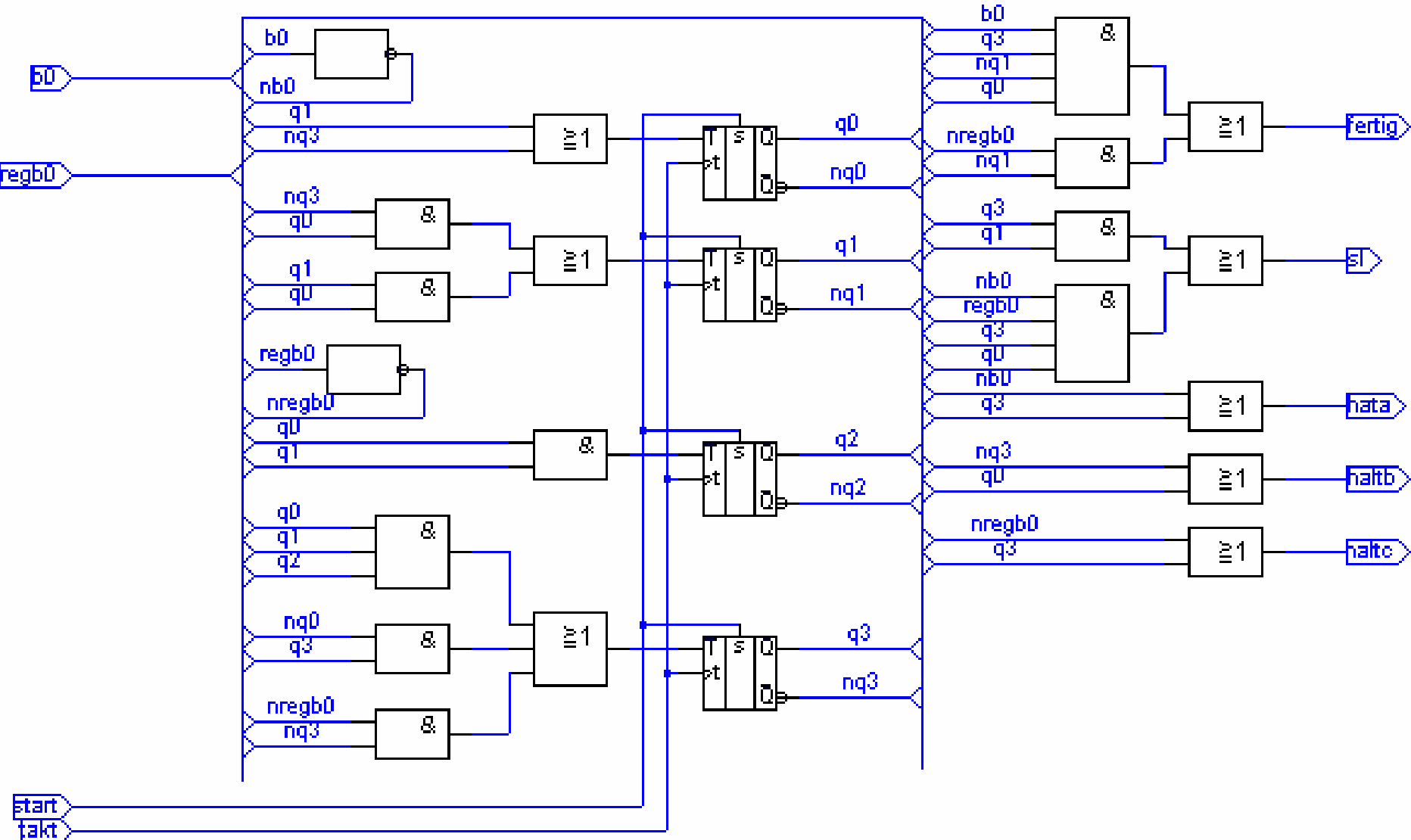

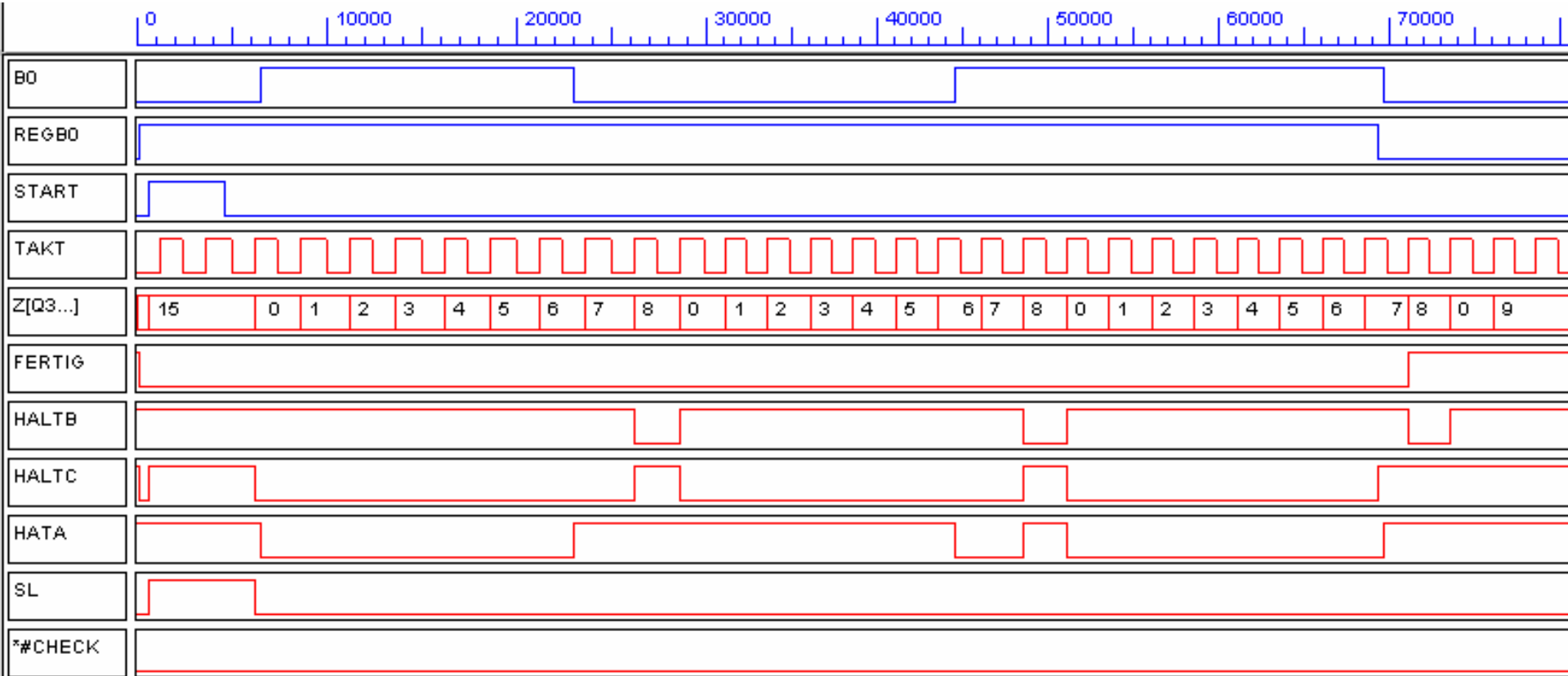

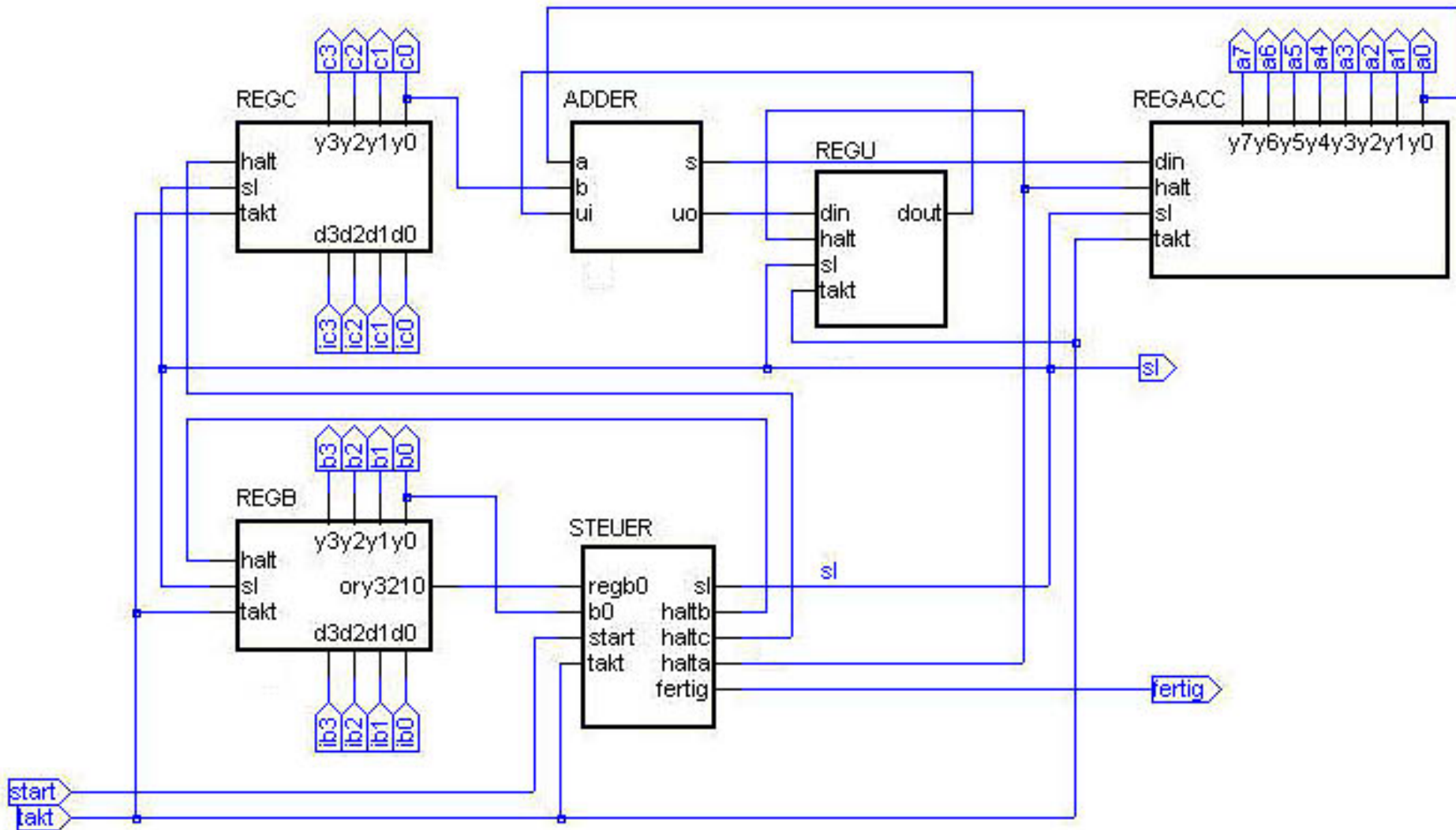

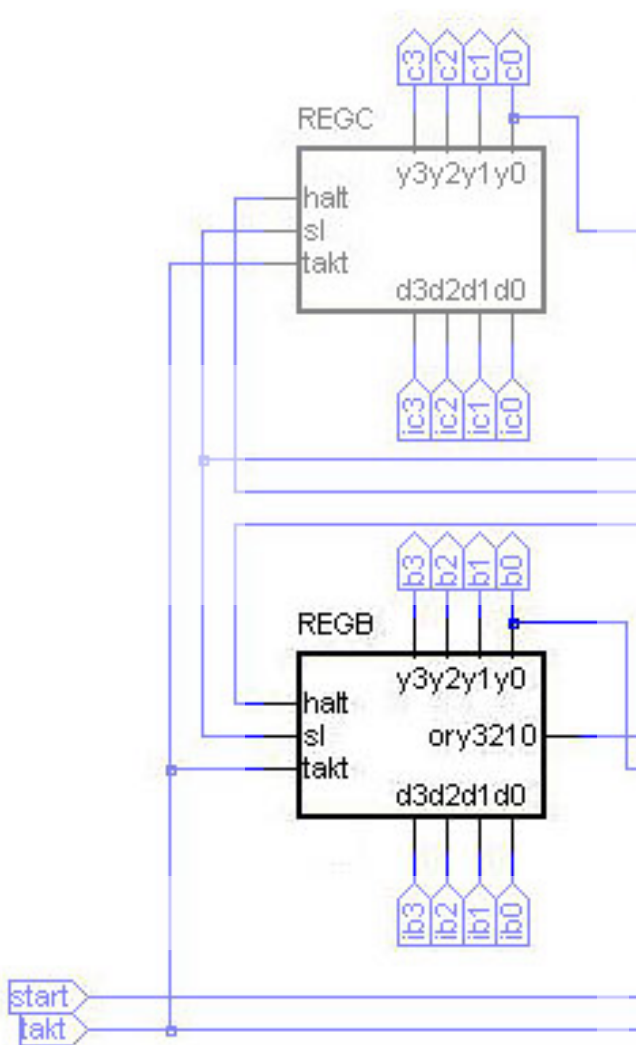

MODULE regb

DECLARATIONS

```
takt      PIN;
sl        PIN;           " 0-schieben 1-laden"
halt      PIN;           " 0-run      1-halt"
ory3210   PIN;           " 0 wenn regb==0
d3..d0    PIN;           " Dateneingaenge "
y3..y0    PIN ISTYPE 'reg'; " Schieberegister "
```

```
Q        = [y3..y0];
QS       = [0,y3..y1];
QL       = [d3..d0];
```


EQUATIONS


```
Q.clk    = takt;


ory3210  = y3 # y2 # y1 # y0;
```


```
WHEN (sl==0) THEN WHEN (halt==1) THEN Q=Q;
                                     ELSE Q=QS;
                                     ELSE Q=QL;
```

END

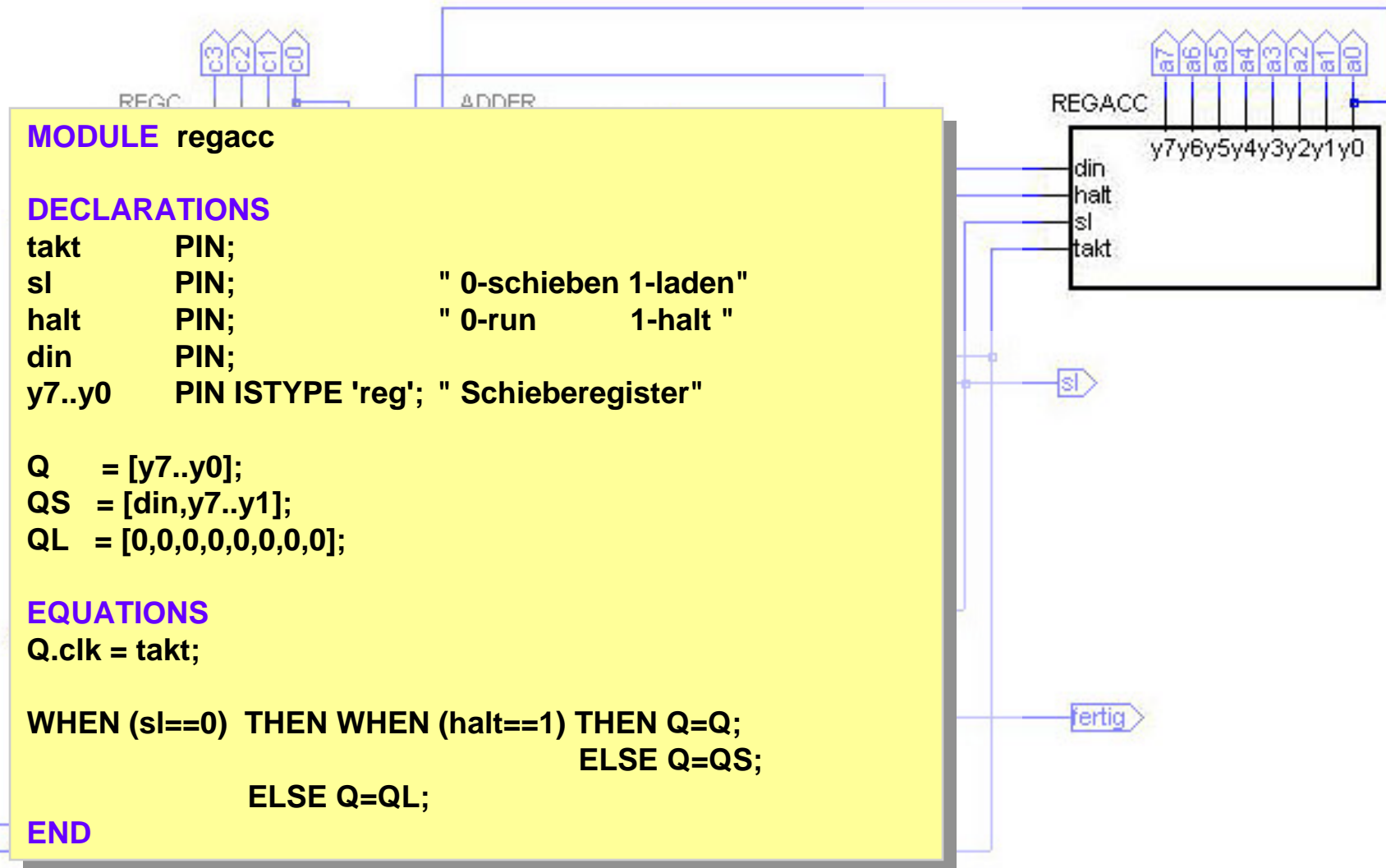

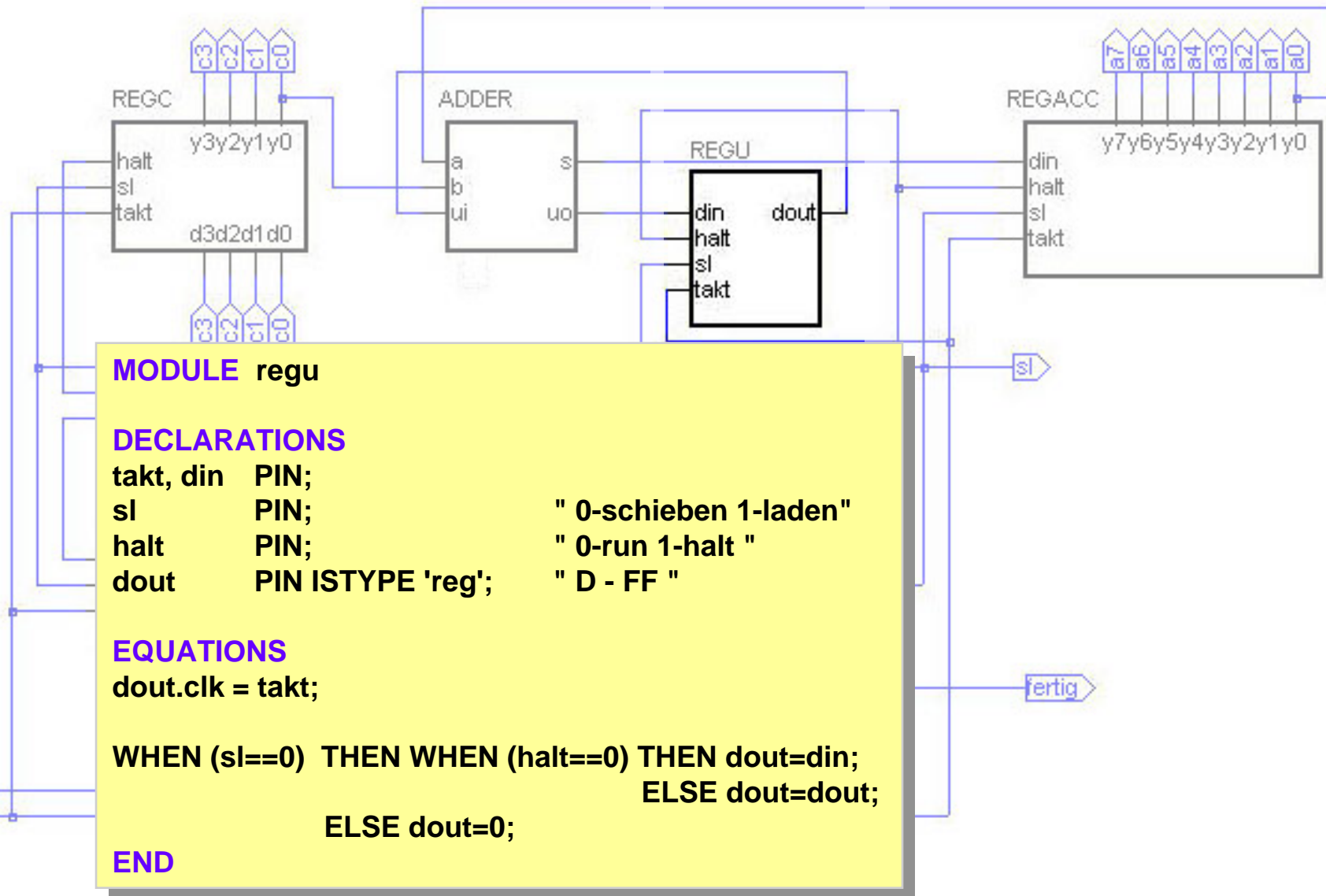

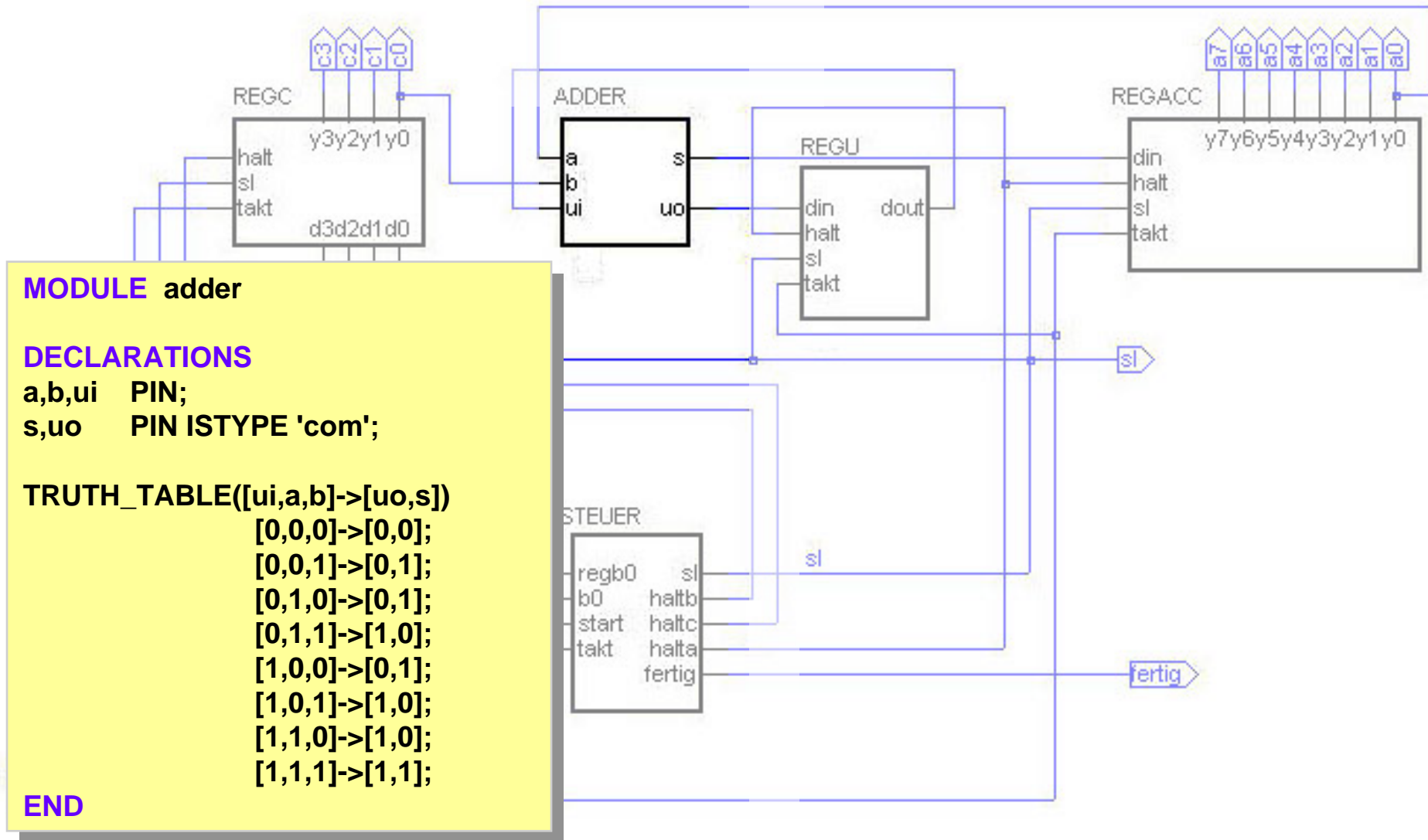

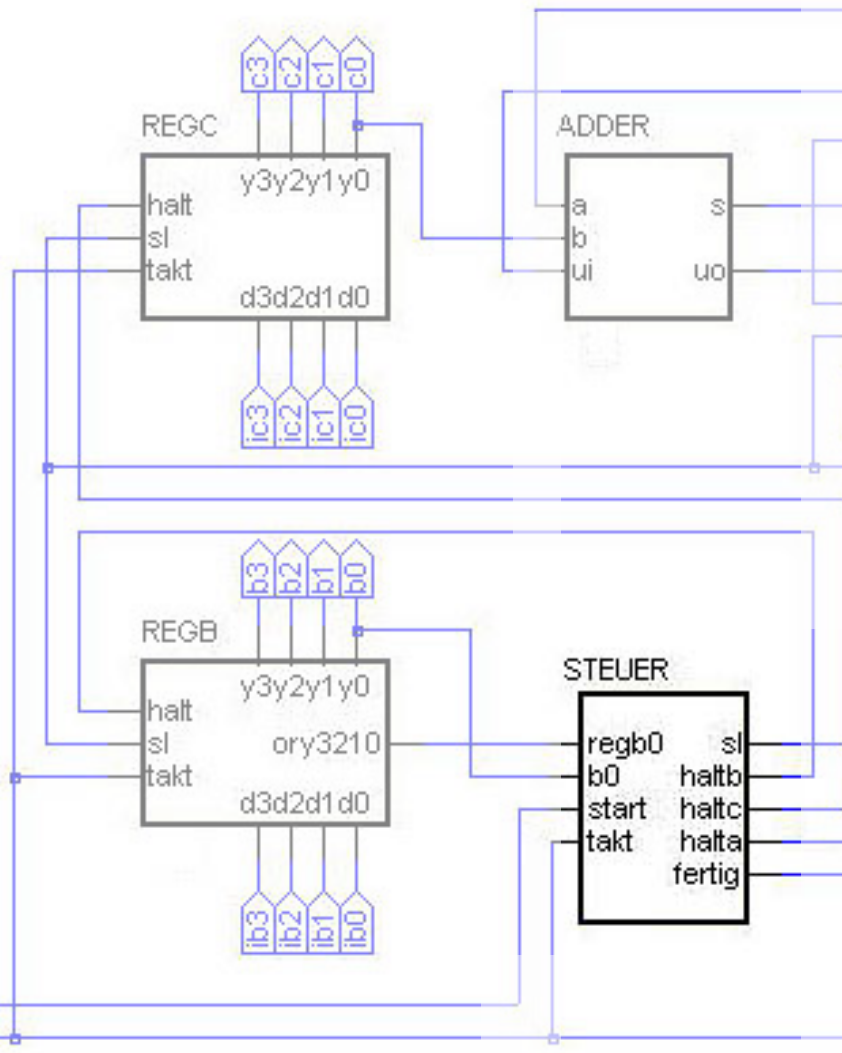

MODULE steuer

DECLARATIONS

```
takt      PIN;
regb0    PIN;
b0       PIN;
start    PIN;
sl       PIN ISTYPE 'com';
halta    PIN ISTYPE 'com';
haltb    PIN ISTYPE 'com';
haltc    PIN ISTYPE 'com';
fertig   PIN ISTYPE 'com';
q3..q0  NODE ISTYPE 'reg';
```

Z = [q3,q2,q1,q0];

EQUATIONS

```
Z.clk = takt;
Z.ap  = start;
q0.t  = !q3 # q1;
q1.t  = !q3 & q0 # q1 & q0;
q2.t  = q1 b0 & q3 & !q1 & q0 # !regb0 & !q1;
sl    = !b0 & q0 ;
q3.t  = q3 & !q0 # !regb0 & !q3 # q2 & q1 & q0;
fertig = & regb0 & q3 & q0 # q3 & q1;
halta  = !b0 # q3;
haltb  = !q3 # q0;
haltc  = !regb0 # q3;
```

END

 

```

MODULE steuer
DECLARATIONS
Takt, start  PIN;
Regb0, b0   PIN;
sl          PIN ISTYPE 'com';
halta      PIN ISTYPE 'com';
haltb      PIN ISTYPE 'com';
haltc      PIN ISTYPE 'com';
fertig     PIN ISTYPE 'com';
q3..q0     NODE ISTYPE 'reg';

" ---Eingangsbuchstaben--- "
X          = [b0,regb0];
X0 MACRO {(X == [0,0])};
X1 MACRO {(X == [0,1])};
X3 MACRO {(X == [1,1])};

" ---Zustandsbuchstaben--- "
Z          = [q3,q2,q1,q0];
Z0         = [0,0,0,0];
..
Z15        = [1,1,1,1];

" ---Ausgangsbuchstaben--- "
Y          = [fertig,sl,halta,haltb,haltc];
Ystart    MACRO {Y=[0,1,1,1,1]};
Yfertig    MACRO {Y=[1,0,1,1,1]};
Yb         MACRO {Y=[0,0,1,0,1]};
Yc         MACRO {Y=[0,0,1,1,0]};
Yac        MACRO {Y=[0,0,0,1,0]};
    
```



EQUATIONS

```

Z.clk = takt;
Z.ap  = start;
    
```

STATE DIAGRAM Z

```

STATE Z0:
    IF X3 THEN Z1 WITH Yac
    IF X1 THEN Z1 WITH Yc
    IF X0 THEN Z9 WITH Yfertig
    
```

```

STATE Z1:
    IF X3 THEN Z2 WITH Yac
    IF X1 THEN Z2 WITH Yc
    
```

```

STATE Z8:
    IF X3 THEN Z0 WITH Yb
    IF X1 THEN Z0 WITH Yb
    
```

```

STATE Z9:
    IF X3 THEN Z9 WITH Yfertig
    IF X1 THEN Z9 WITH Yfertig
    IF X0 THEN Z9 WITH Yfertig
    
```

```

STATE Z15:
    IF X3 THEN Z0 WITH Ystart
    IF X1 THEN Z0 WITH Ystart
    IF X0 THEN Z0 WITH Ystart
    
```

END

